
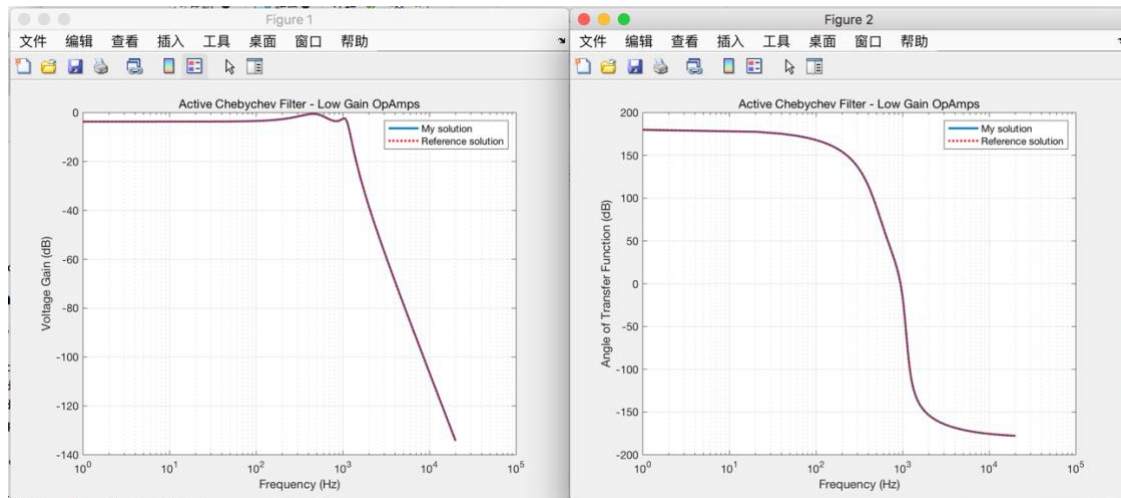



Q1

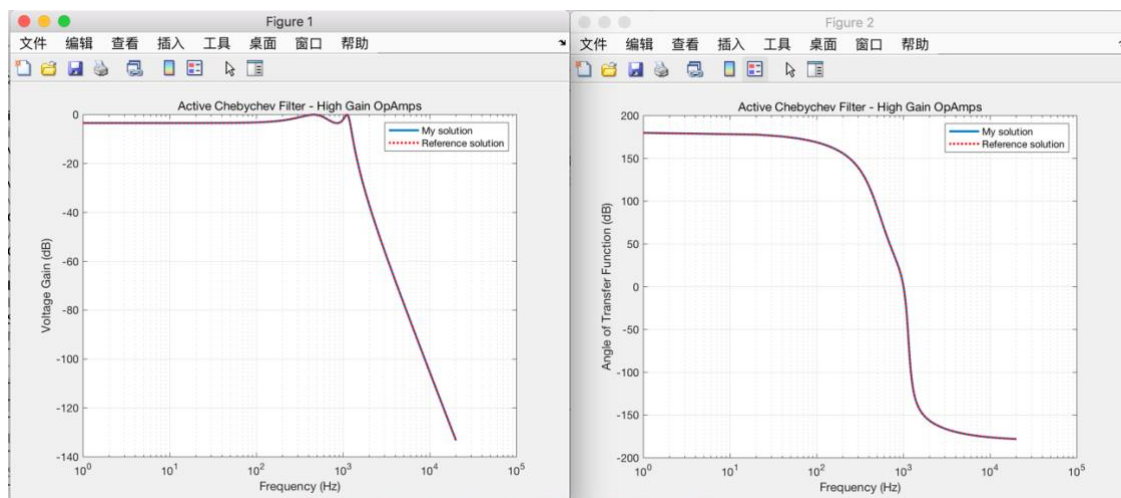


Testbench\_chebychev\_filter




Testbench\_chebychev\_filter\_largeGain.

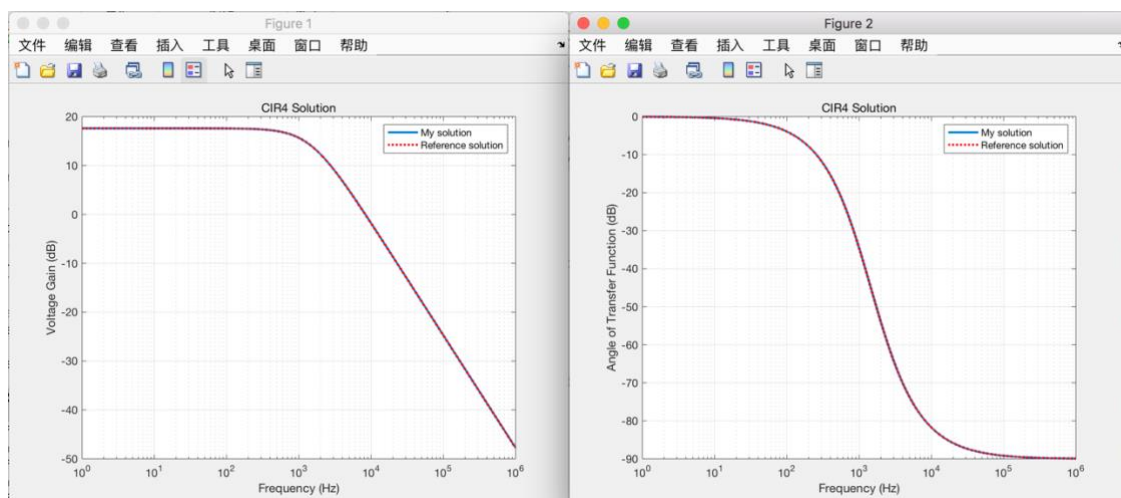


TestBench\_CIR4

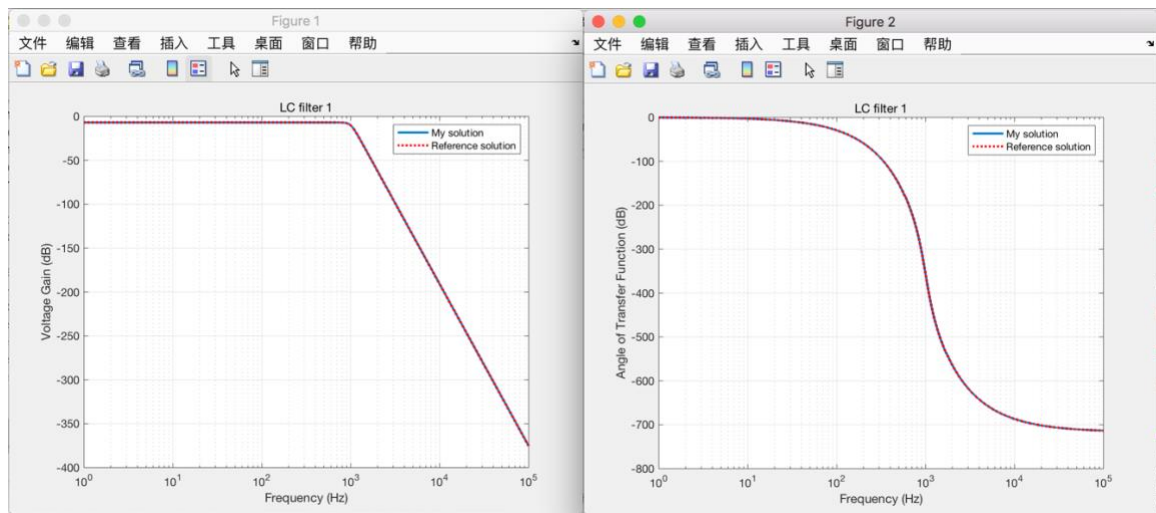

TestBench\_LCfilter1

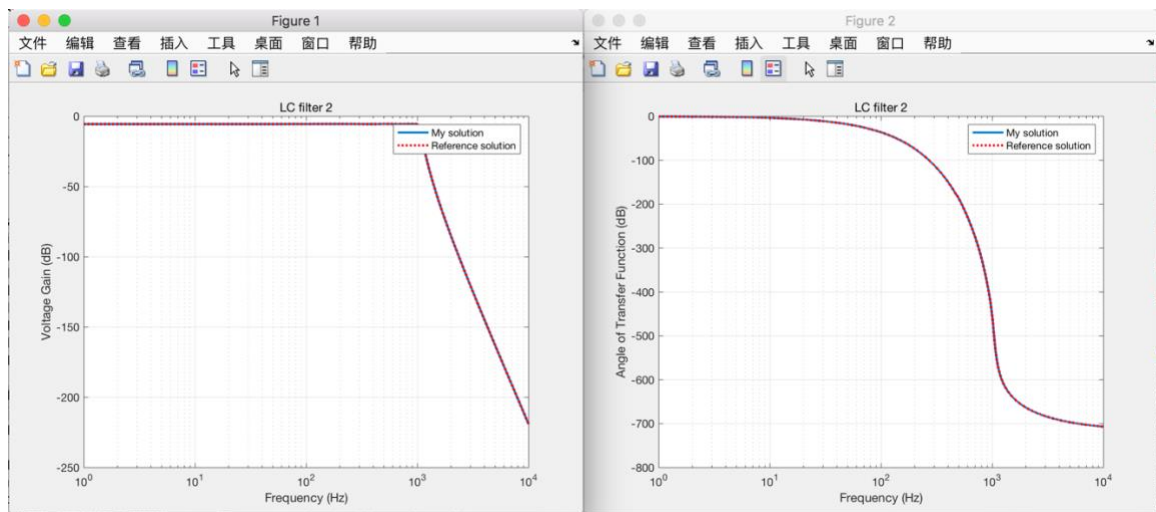


TestBench\_LCfilter2

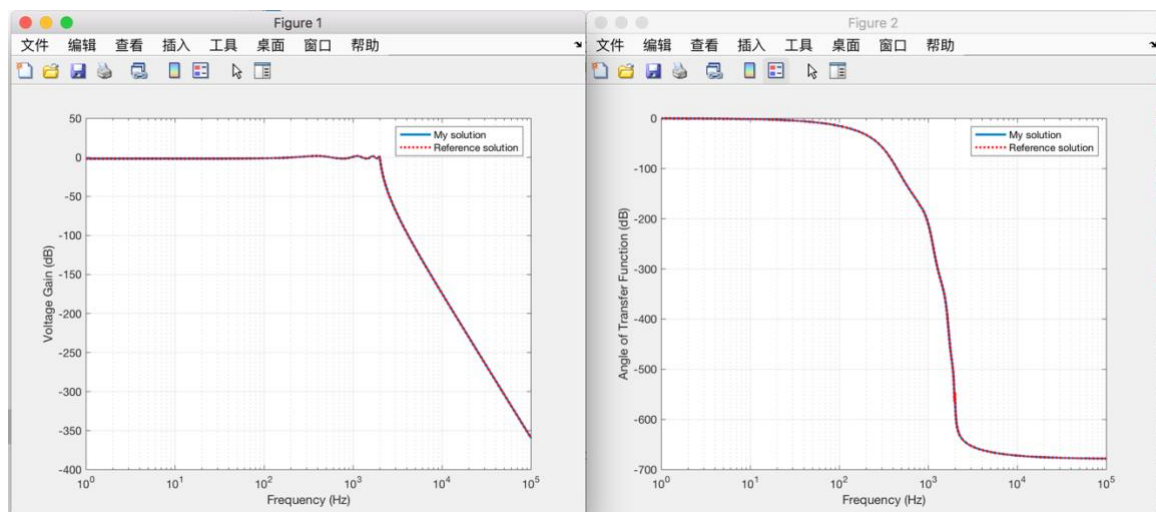


TestBench\_LCfilter3

Q2

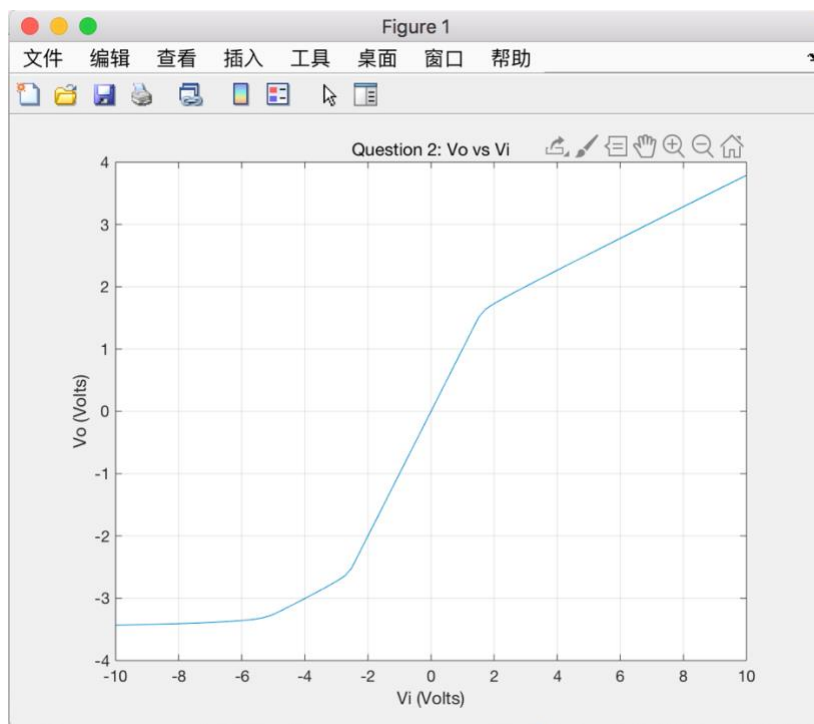


Solutions:

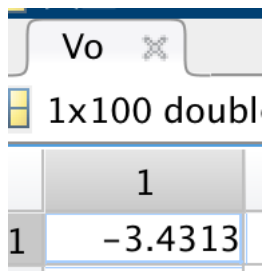

When  $V_I = -10V$ ,  $V_O = -3.4313V$



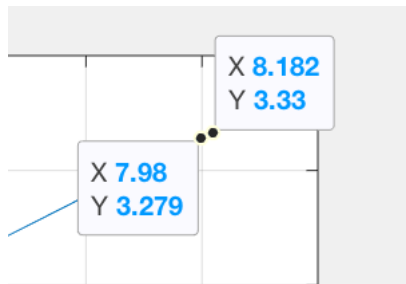This interval is a linear line with a slope 1. In this way, when  $V_I = -2V$ ,  $V_O = -2V$ .



When  $V_I = 8V$ ,  $V_o = 3.279V + (3.33 - 3.279) / (8.182 - 7.98) * 0.2 = \mathbf{3.284V}$